
Acausality

A single component for all causalities

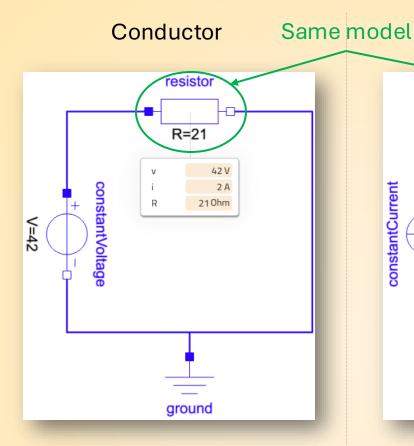

R=21

v 42V
i 2A
R 210hm

ground

Resistor

The resistance R is set
The voltage v is known

→ The current i is the solved for

The resistance R is set
The current i is known

→ The voltage v is the solved

The resistor illustrates well the principle of acausality.

And it is true for all models.

It does not mean that all causalities are desired – there are ways to influence the causality selection.


Dr. Clément Coïc



Bi-causality

All variables known to compute the parameter value

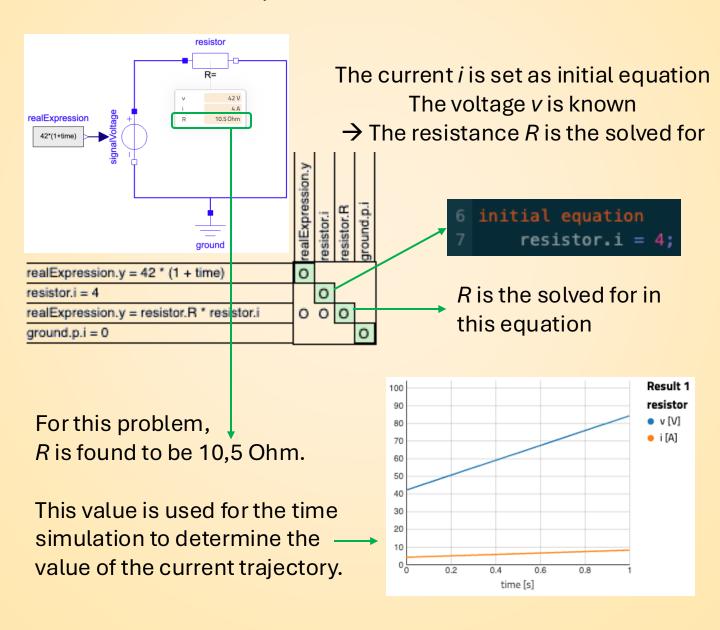In Modelica, a model results in two problems to solve: the initialization problem and the time simulation problem. Here we leverage the former to compute the value of R and reuse the computed value for time simulation.



Dr. Clément Coïc